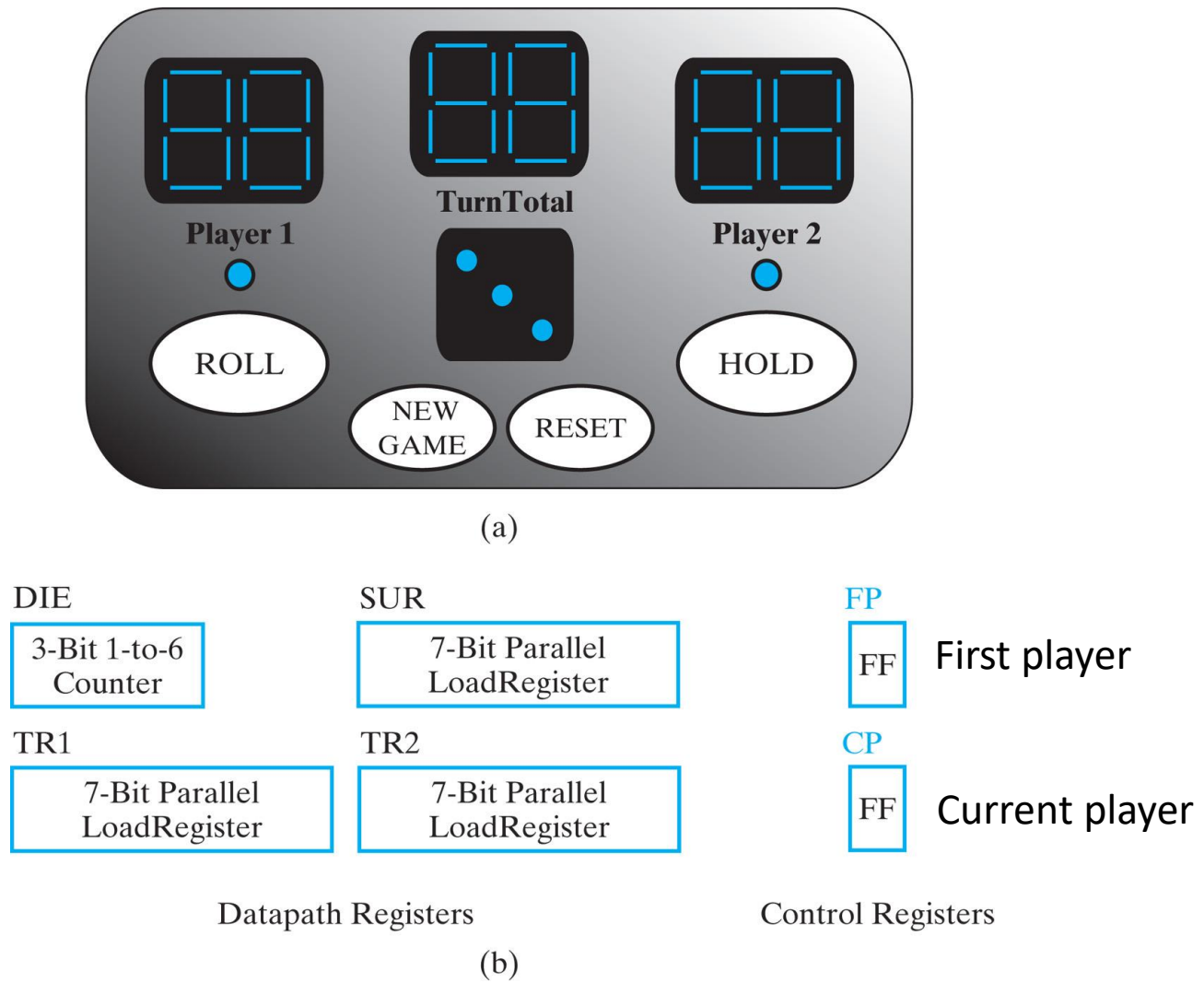


# LAB 2

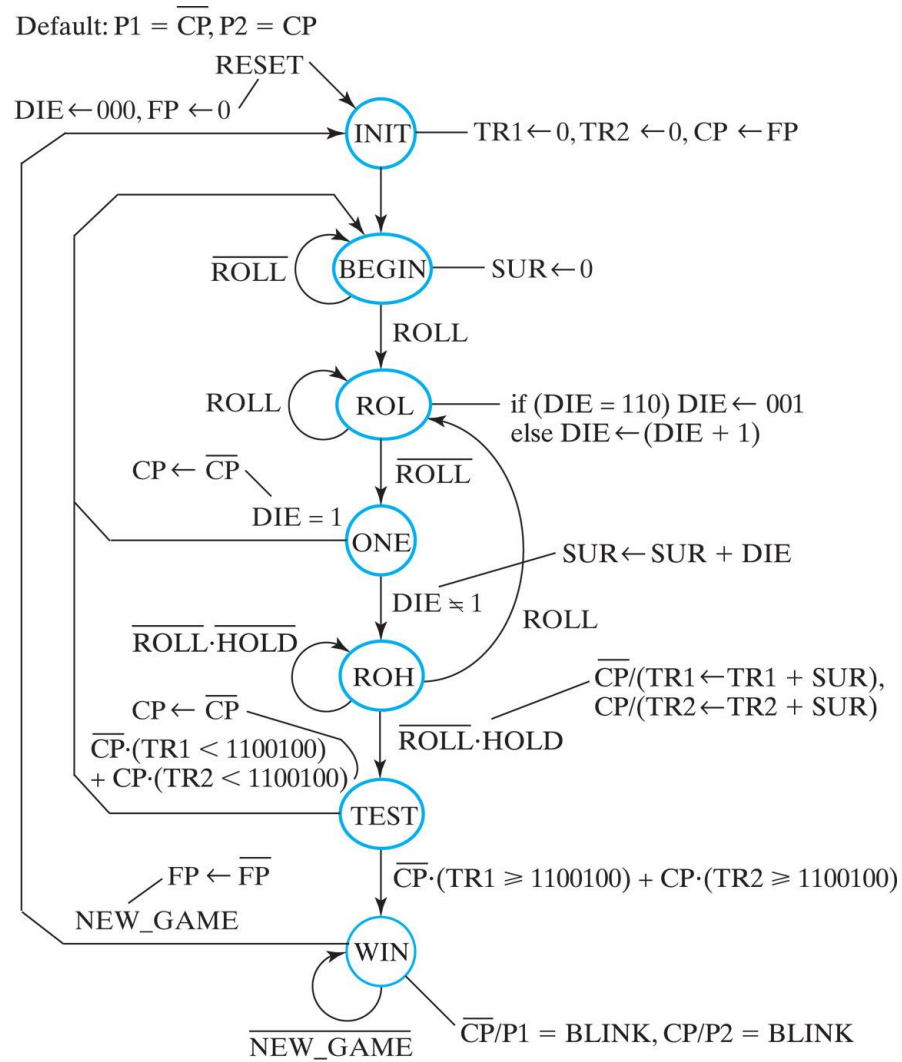
PIG GAME

**FIGURE 6-28** PIG: (a) Exterior View of PIG, (b) PIG Registers




**□ TABLE 6-17**  
**Inputs, Outputs, and Registers of PIG**
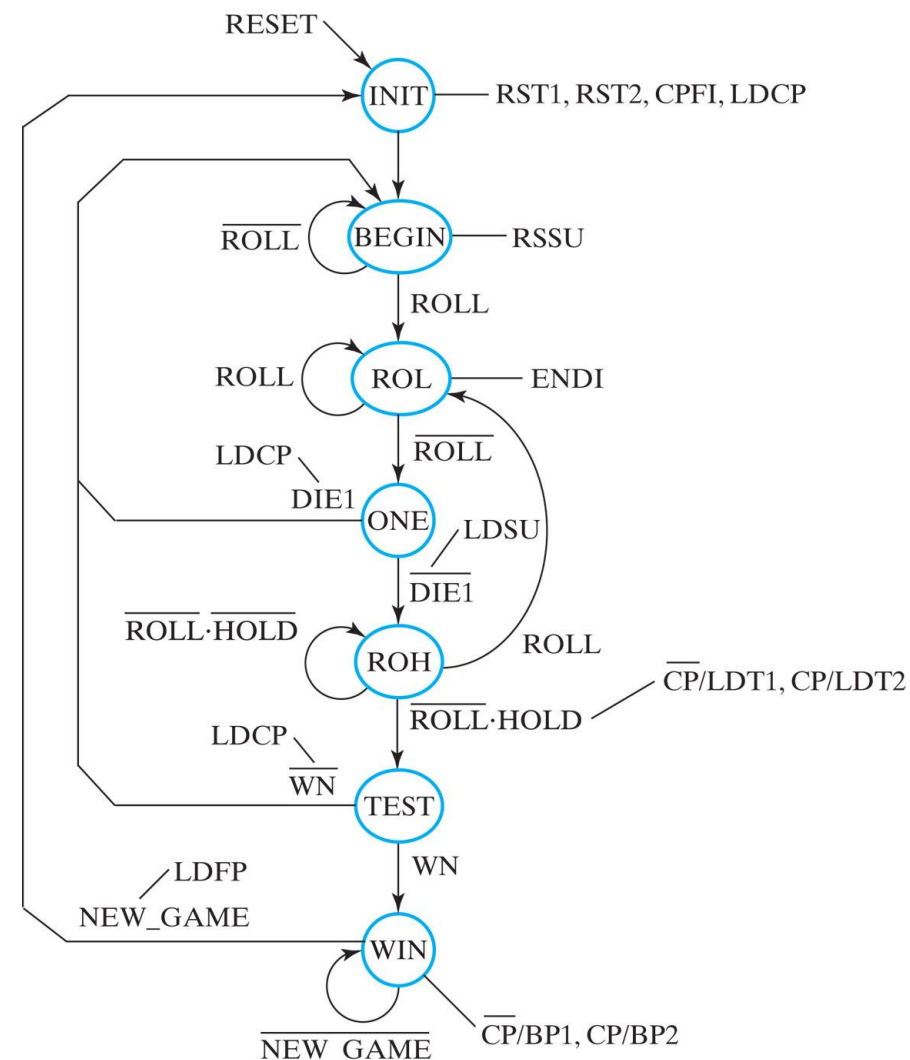
| Symbol   | Name/Function   | Type                      |
|----------|---|---------------------------|
| ROLL     | 1: Starts die rolling, 0: Stops die rolling                       | Control input             |
| HOLD     | 1: Ends player turn, 0: Continues player turn.                    | Control input             |
| NEW_GAME | 1: Starts new game, 0: Continues current game                     | Control input             |
| RESET    | 1: Resets game to INIT state, 0: No action                        | Control input             |
| DDIS     | 7-Bit LED die display array                                       | Data output<br>vector     |
| SUB      | 14-Bit 7-segment pair (a, b, c, d, e, f, g) to Turn Total display | Data output<br>vector     |
| TP1      | 14-Bit 7-segment pair (a, b, c, d, e, f, g) to Player 1 display   | Data output<br>vector     |
| TP2      | 14-Bit 7-segment pair (a, b, c, d, e, f, g) to Player 2 display   | Data output<br>vector     |
| P1       | 1: Player 1 LED on, 0: Player 1 LED off                           | Data output               |
| P2       | 1: Player 2 LED on, 0: Player 2 LED off                           | Data output               |
| DIE      | Die value—specialized counter to count 1,...,6,1,...              | 3-Bit data register       |
| SUR      | Subtotal for active player—parallel load register                 | 7-Bit data register       |
| TR1      | Total for Player 1—parallel load register                         | 7-Bit data register       |
| TR2      | Total for Player 2—parallel load register                         | 7-Bit data register       |
| FP       | First player—flip-flop 0: Player 1, 1: Player 2                   | 1-Bit control<br>register |
| CP       | Current player—flip-flop 0: Player 1, 1: Player 2                 | 1-Bit control<br>register |

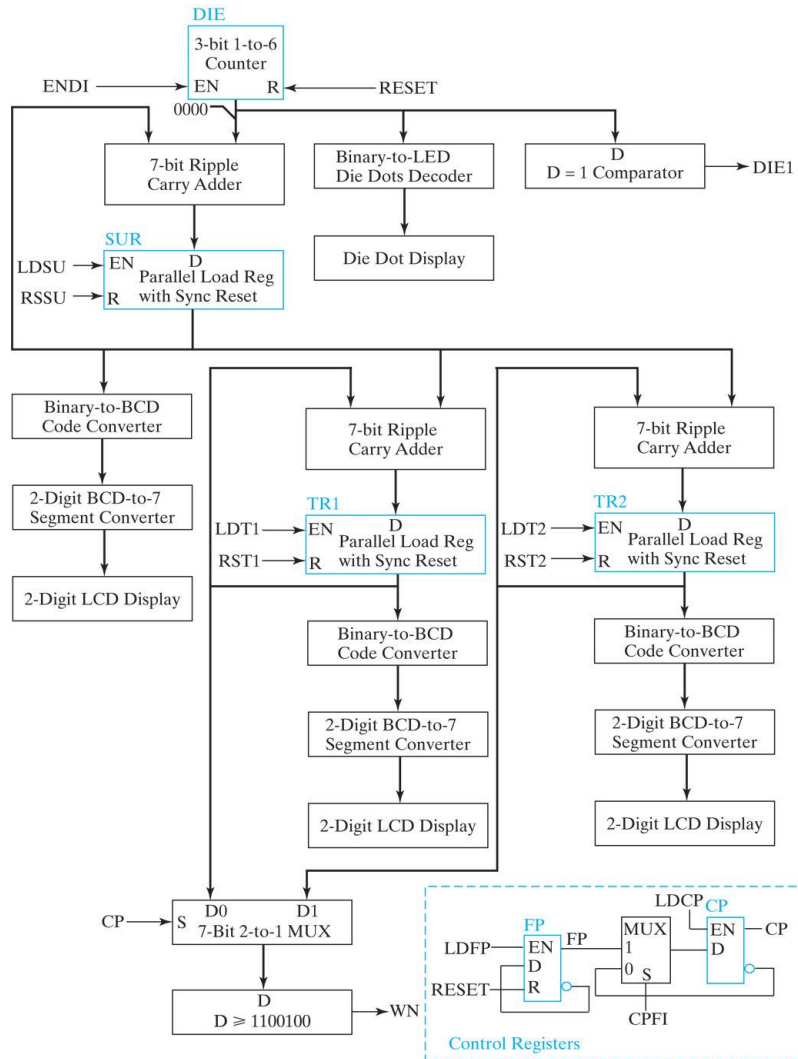



**TABLE 6-18**  
**Datapath Output Actions and Control and Status Signals for PIG**

| Action or Status  | Control or Status Signals | Meaning for Values 1 and 0  |
|---|---------------------------|---|
| $TR1 \leftarrow 0$<br>$TR1 \leftarrow TR1 + SUR$  | RST1<br>LDT1              | 1: Reset TR1 (synchronous reset), 0: No action<br>1: Add SUR to TR1, 0: No action         |
| $TR2 \leftarrow 0$<br>$TR2 \leftarrow TR2 + SUR$  | RST2<br>LDT2              | 1: Reset TR2 (synchronous reset), 0: No action<br>1: Add SUR to TR2, 0: No action         |
| $SUR \leftarrow 0$<br>$SUR \leftarrow SUR + DIE$  | RSSU<br>LDSU              | 1: Reset SUR (synchronous reset), 0: No action<br>1: Add DIE to SUR, 0: No action         |
| $DIE \leftarrow 000$<br>if ( $DIE = 110$ )<br>$DIE \leftarrow 001$<br>else $DIE \leftarrow DIE + 1$ | RESET<br>ENDI             | 1: Reset DIE to 000 (asynchronous reset)<br>1: Enable DIE to increment, 0: Hold DIE value |
| $P1 = BLINK$  | BP1                       | 1: Connect P1 to BLINK, 0: Connect P1 to 1  |




# What are the inputs and outputs?



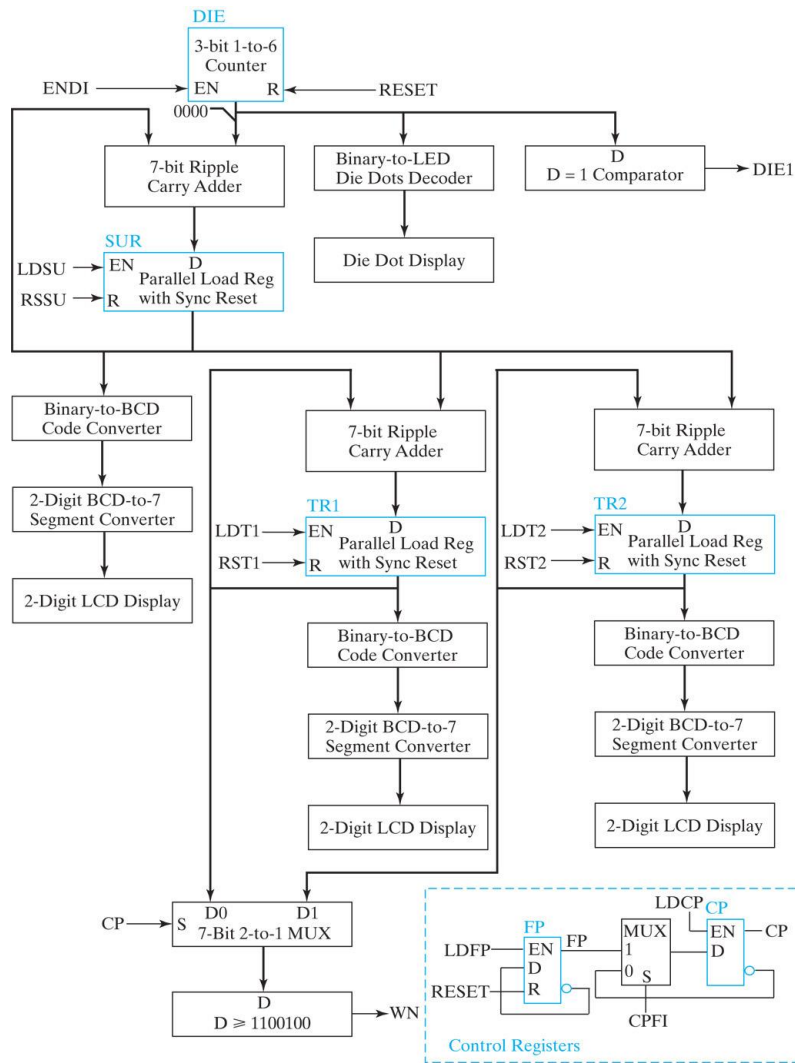



Copyright ©2016 Pearson Education, All Rights Reserved



|           |        |        |                                |
|-----------|--------|--------|--------------------------------|
| std_logic | clock  | CP     | std_logic                      |
| std_logic | reset  | FP     | std_logic                      |
| std_logic | ENADIE | DIGIT0 | std_logic_vector( 3 downto 0 ) |
| std_logic | LDSU   | DIGIT1 | std_logic_vector( 3 downto 0 ) |
| std_logic | LDT1   | DIGIT2 | std_logic_vector( 3 downto 0 ) |
| std_logic | LDT2   | DIGIT3 | std_logic_vector( 3 downto 0 ) |
| std_logic | RSSU   | LEDDIE | std_logic_vector(2 downto 0)   |
| std_logic | RST1   | DIE1   | std_logic                      |
| std_logic | RST2   | WN     | std_logic                      |

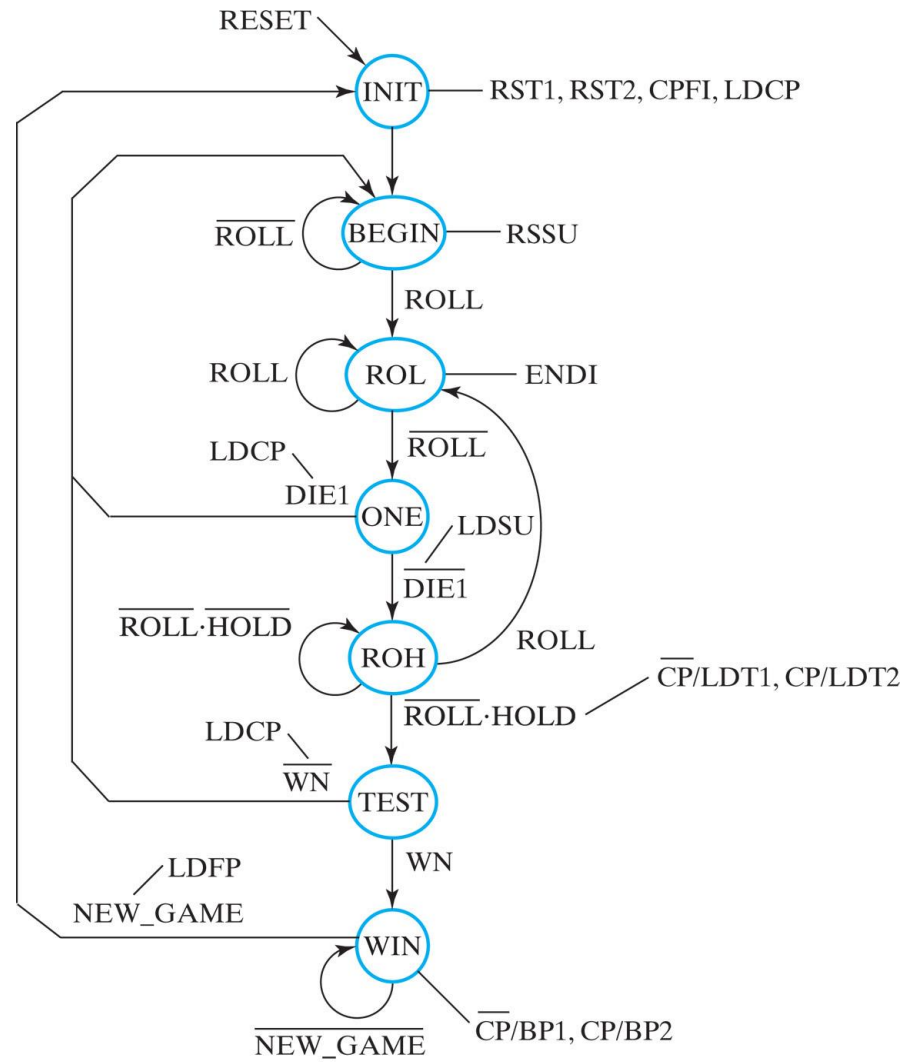

What are the inputs and outputs?



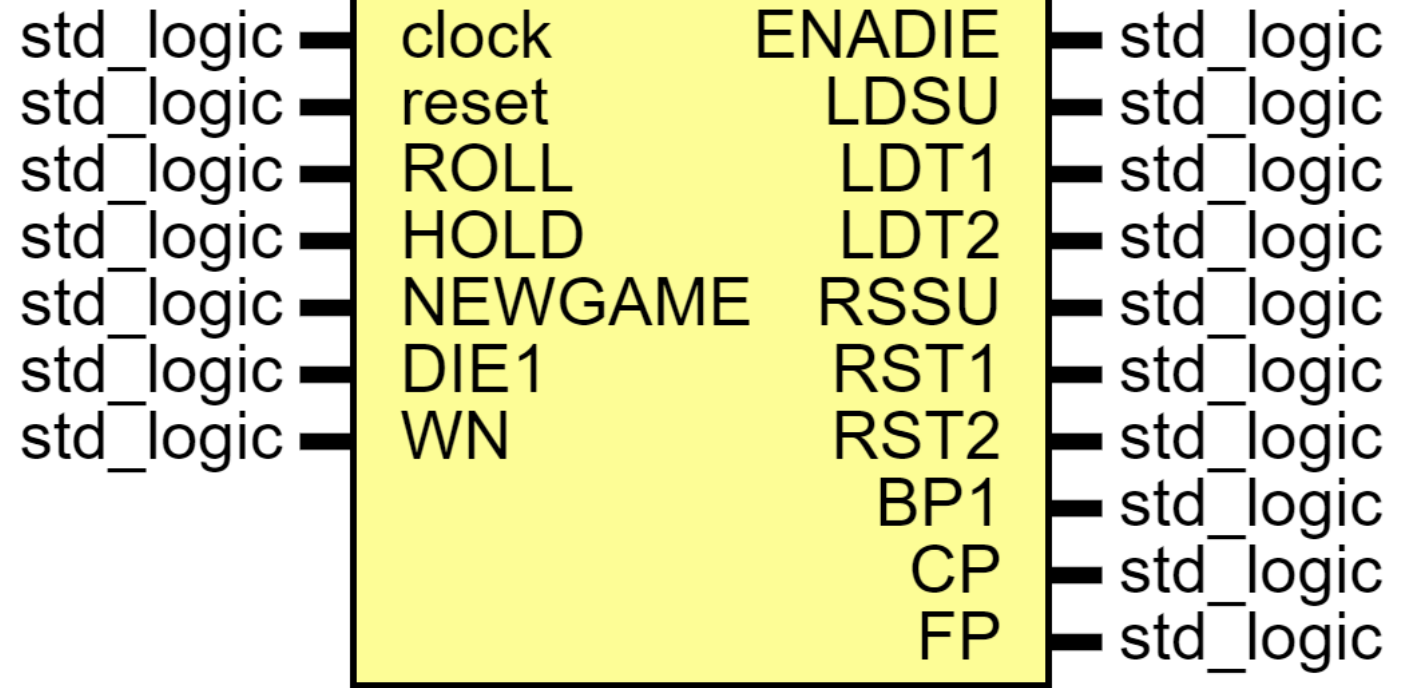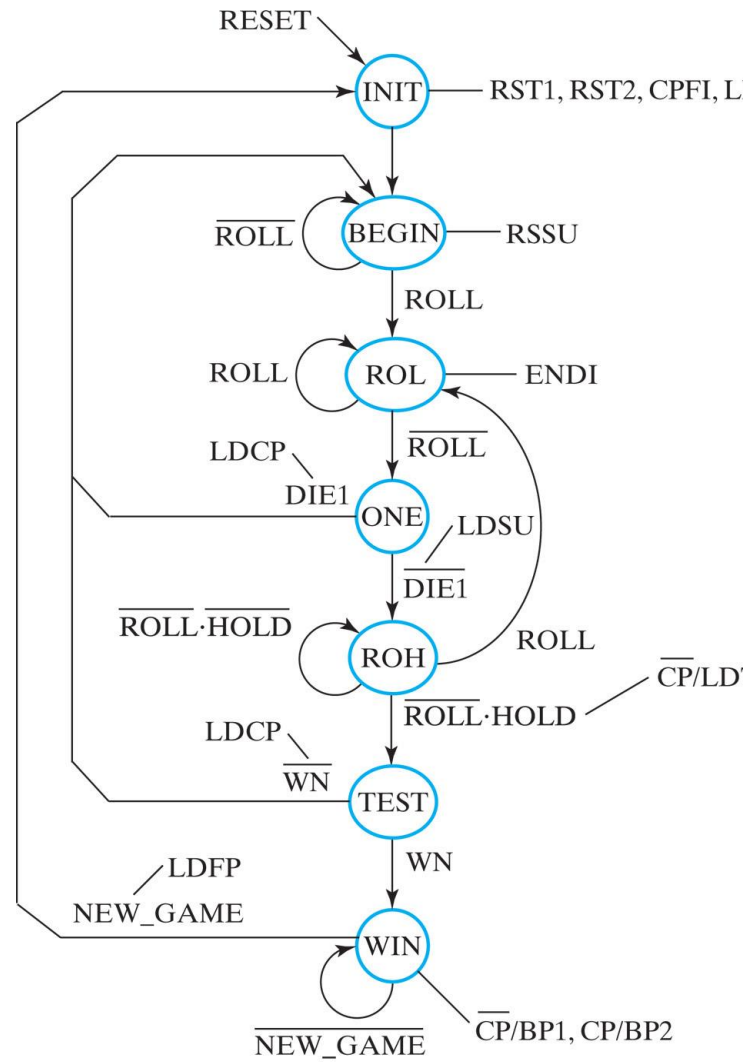

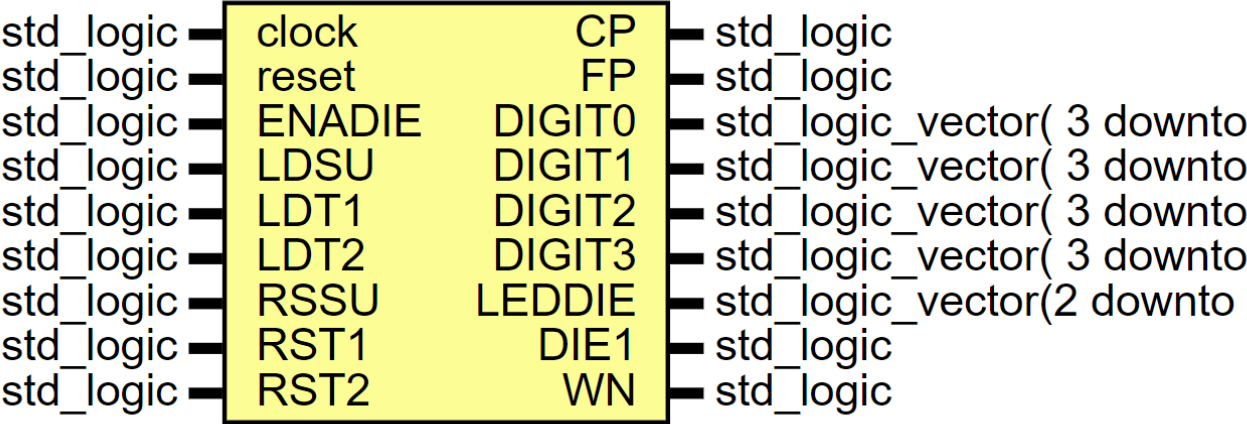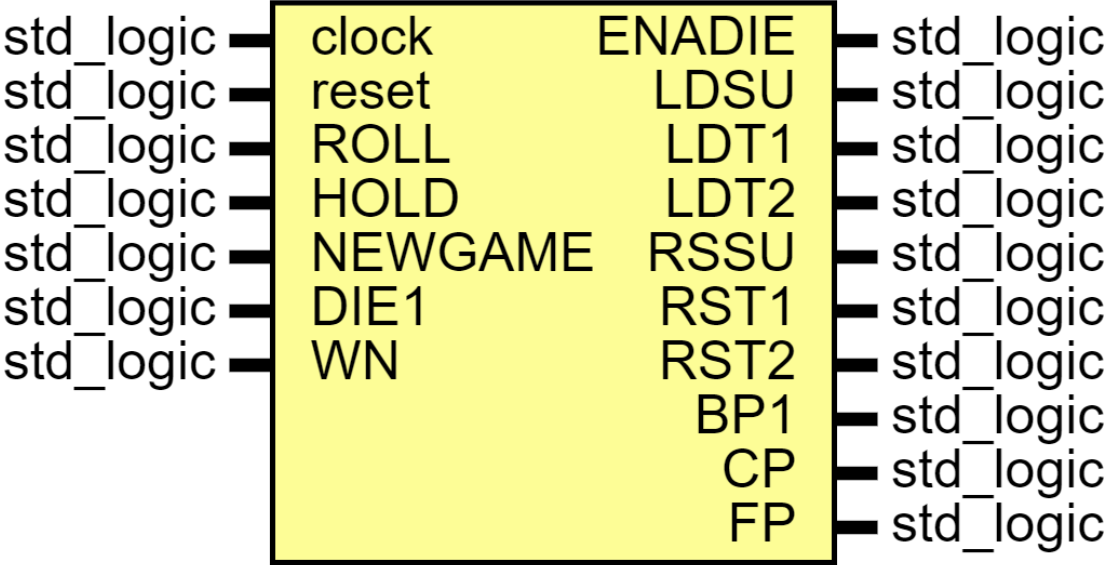

entity datapath is

port(

clock : in std\_logic; *--! Clock*

reset : in std\_logic; *--! Reset*

ENADIE : in std\_logic; *--! Enable Die to increment*

LDSU : in std\_logic; *--! Add DIE to SUR register*

LDT1 : in std\_logic; *--! Add SUR to TR1 register*

LDT2 : in std\_logic; *--! Add SUR to TR2 register*

RSSU : in std\_logic; *--! Reset SUR register*

RST1 : in std\_logic; *--! Reset TR1 register*

RST2 : in std\_logic; *--! Reset TR2 register*

CP : **inout** std\_logic; *--! current player (register outside)*

FP : **inout** std\_logic; *--! First player (register outside)*

DIGIT0 : out std\_logic\_vector( 3 downto 0 ); *--! digit to the right*

DIGIT1 : out std\_logic\_vector( 3 downto 0 ); *--! 2nd digit to the left*

DIGIT2 : out std\_logic\_vector( 3 downto 0 ); *--! 3rd digit to the left*

DIGIT3 : out std\_logic\_vector( 3 downto 0 ); *--! digit to the left*


LEDDIE : out std\_logic\_vector(2 downto 0); *--! LEDs to display the die value*

DIE1 : out std\_logic; *--! signal that a one has been obtained*

WN : out std\_logic; *--! WIN has been achieved by a player*

);

end entity datapath;

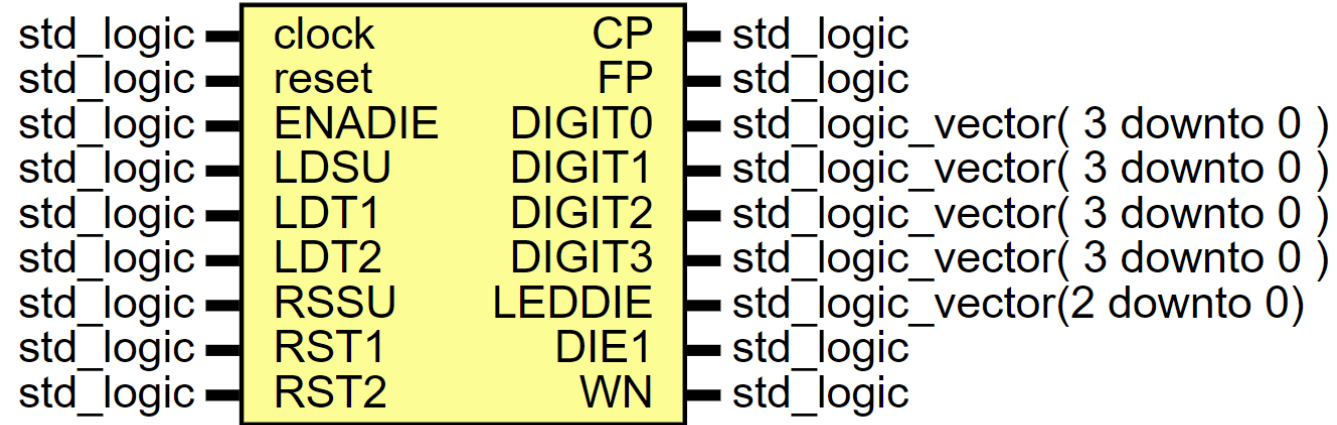


# DATAPATH

```

Main_process : process(clock,reset) begin
  if reset = '1' then
    -- reset
    DIE <= (others => '0'); --! asynchronous reset
  else
    if rising_edge(clock) then
      if RST1 = '1' then
        TR1 <= (others => '0');
      end if;
      if RST2 = '1' then
        TR2 <= (others => '0');
      end if;
      if RSSU = '1' then
        SUR <= (others => '0');
      end if;
      if LDT1 = '1' then
        TR1 <= TR1 + SUR;
      end if;
      if LDT2 = '1' then
        TR2 <= TR2 + SUR;
      end if;
      if ENADIE = '1' then
        case DIE is
          when "110" => DIE <= "001";
          when others => DIE <= DIE + 1;
        end case;
      end if;
    end if;
  end if;
end process;

```




```

if DIE = "001" then
  DIE1 <= '1';
else
  DIE1 <= '0';
end if;
if LDSU = '1' then
  SUR <= SUR + (frontbits & DIE);
end if;
if CP = '1' then
  D <= TR2;
else
  D <= TR1;
end if;

if (D > "1100011") then
  WN <= '1';
else
  WN <= '0';
end if;

end if;
end if;
--! connection to displays
LEDDIE <= DIE;
DIGIT0 <= bcd1;
DIGIT1 <= bcd2;
DIGIT2 <= bcd3;
DIGIT3 <= bcd4;
end process;

```

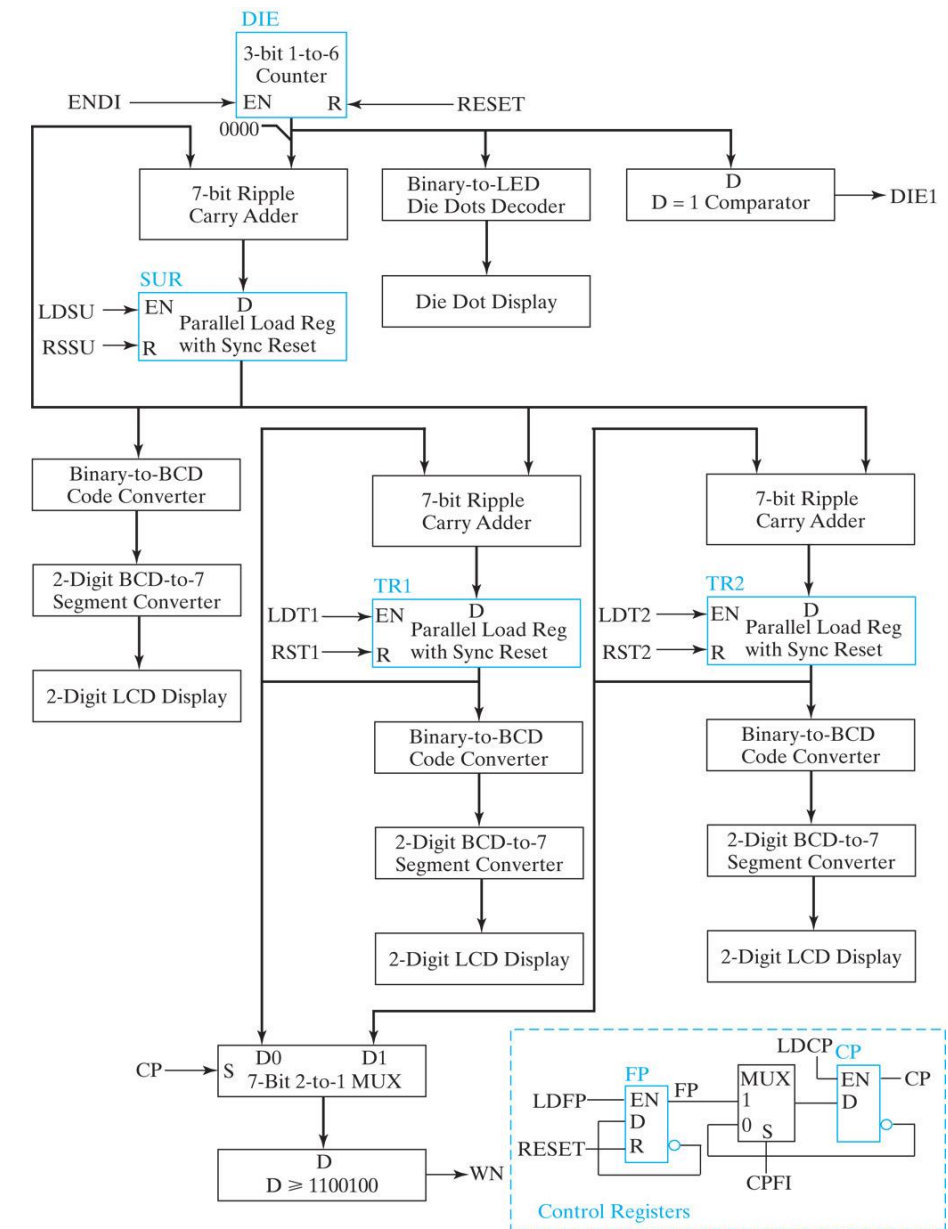




```

Main_process : process(clock,reset) begin
  if reset = '1' then
    -- reset
    DIE <= (others => '0'); --! asynchronous reset
  else
    if rising_edge(clock) then
      if RST1 = '1' then
        TR1 <= (others => '0');
      end if;
      if RST2 = '1' then
        TR2 <= (others => '0');
      end if;
      if RSSU = '1' then
        SUR <= (others => '0');
      end if;
      if LDT1 = '1' then
        TR1 <= TR1 + SUR;
      end if;
      if LDT2 = '1' then
        TR2 <= TR2 + SUR;
      end if;
      if ENADIE = '1' then
        case DIE is
          when "110" => DIE <= "001";
          when others => DIE <= DIE + 1;
        end case;
      end if;
    end if;
  end if;
end process;

```



```

if DIE ="001" then
  DIE1 <= '1';
else
  DIE1 <= '0';
end if;

if LDSU = '1' then
  SUR <= SUR + (frontbits & DIE);
end if;


if CP ='1' then
  D <= TR2;
else
  D <= TR1;
end if;

if (D > "1100011") then
  WN <= '1';
else
  WN <= '0';
end if;

end if;

--! connection to displays
LEDDIE <= DIE;
DIGIT0 <= bcd1;
DIGIT1 <= bcd2;
DIGIT2 <= bcd3;
DIGIT3 <= bcd4;
end process;

```

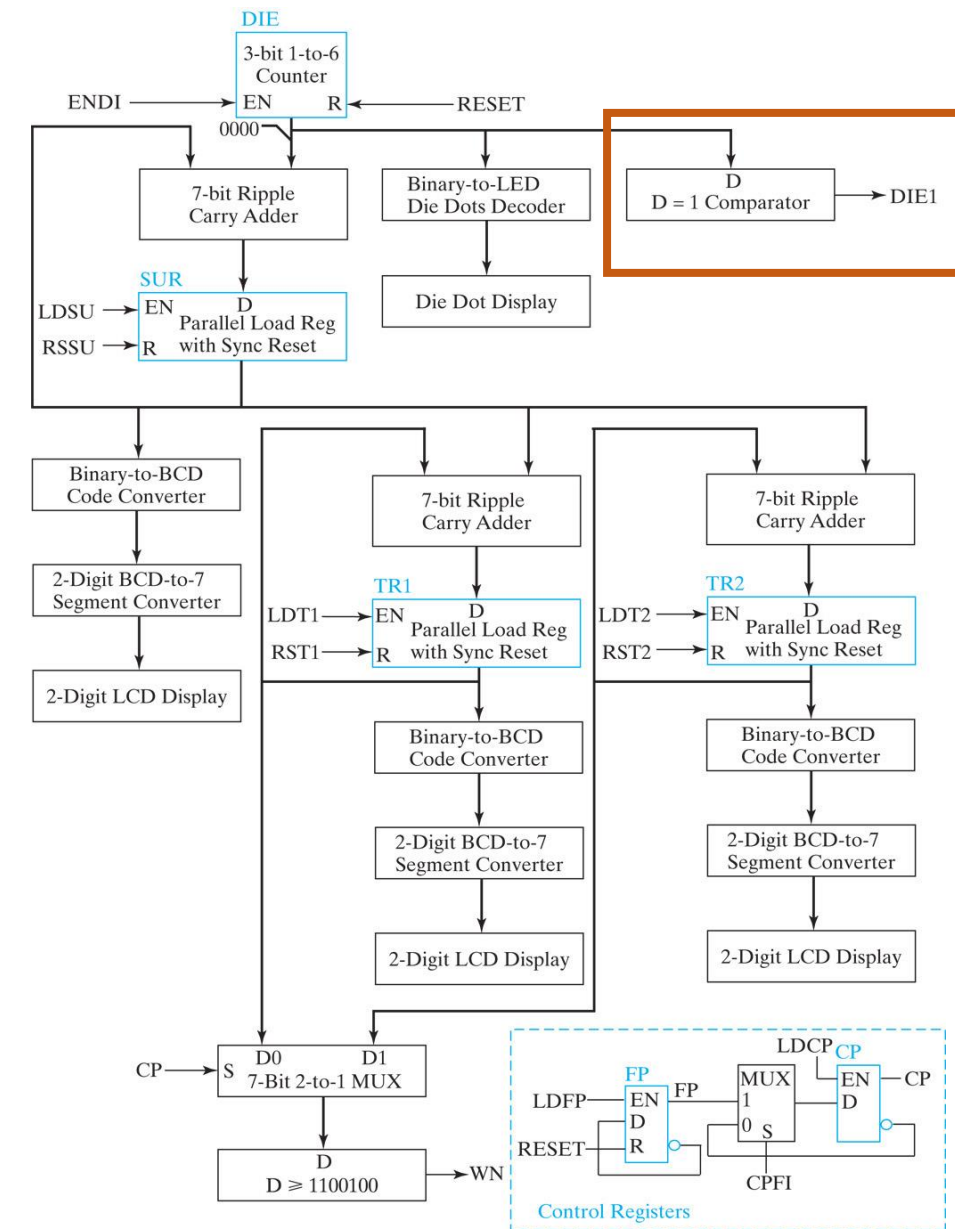




```

Main_process : process(clock,reset) begin
  if reset = '1' then
    -- reset
    DIE <= (others => '0'); --! asynchronous reset
  else
    if rising_edge(clock) then
      if RST1 = '1' then
        TR1 <= (others => '0');
      end if;
      if RST2 = '1' then
        TR2 <= (others => '0');
      end if;
      if RSSU = '1' then
        SUR <= (others => '0');
      end if;
      if LDT1 = '1' then
        TR1 <= TR1 + SUR;
      end if;
      if LDT2 = '1' then
        TR2 <= TR2 + SUR;
      end if;
      if ENADIE = '1' then
        case DIE is
          when "110" => DIE <= "001";
          when others => DIE <= DIE + 1;
        end case;
      end if;
    end if;
  end if;
end process;


```



```

if DIE = "001" then
  DIE1 <= '1';
else
  DIE1 <= '0';
end if;
if LDSU = '1' then
  SUR <= SUR + (frontbits & DIE);
end if;
if CP = '1' then
  D <= TR2;
else
  D <= TR1;
end if;
if (D > "1100011") then
  WN <= '1';
else
  WN <= '0';
end if;
end if;
end if;
--! connection to displays
LEDDIE <= DIE;
DIGIT0 <= bcd1;
DIGIT1 <= bcd2;
DIGIT2 <= bcd3;
DIGIT3 <= bcd4;
end process;


```

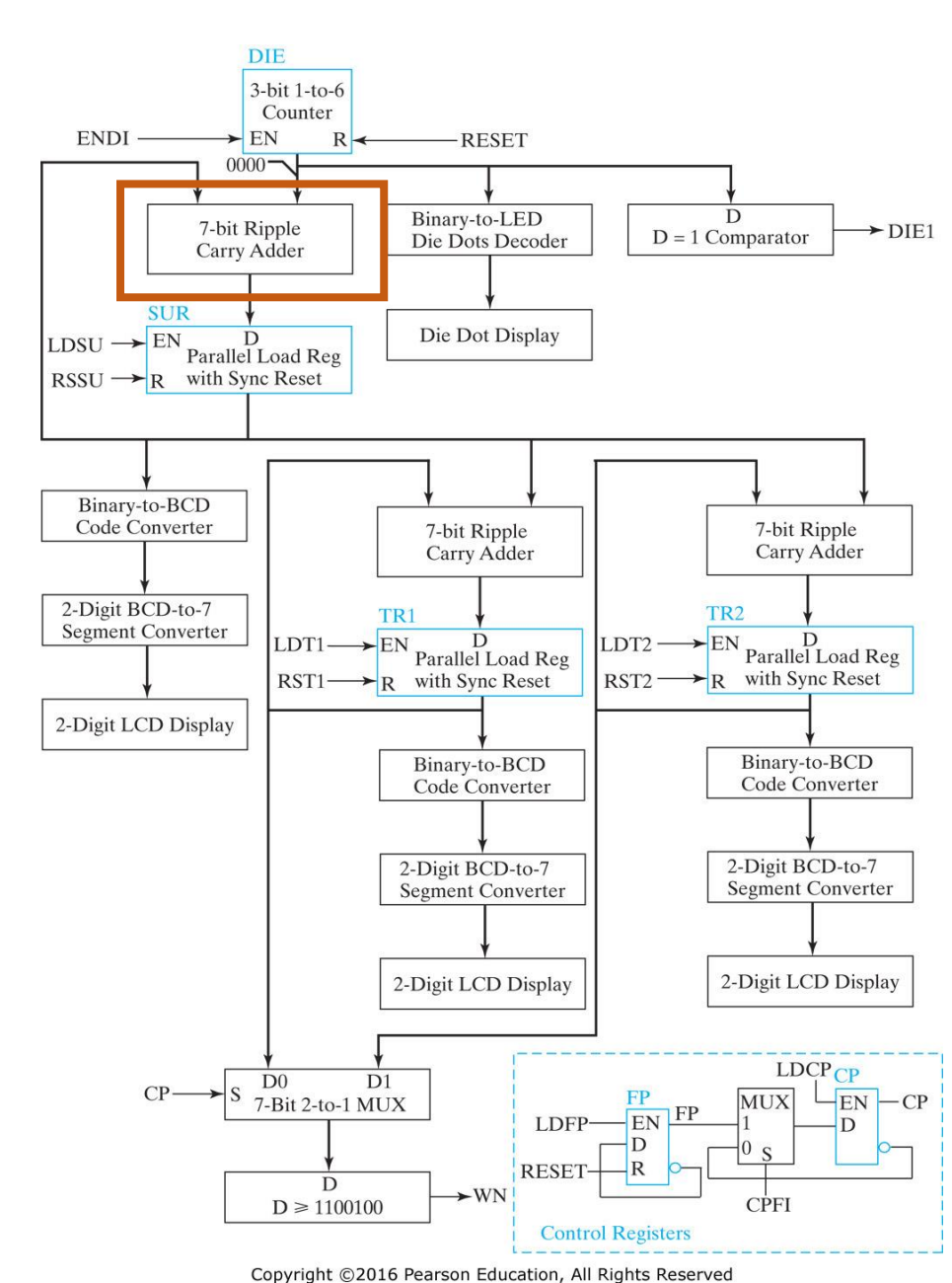

```

Main_process : process(clock,reset) begin
  if reset = '1' then
    -- reset
    DIE <= (others => '0'); --! asynchronous reset
  else
    if rising_edge(clock) then
      if RST1 = '1' then
        TR1 <= (others => '0');
      end if;
      if RST2 = '1' then
        TR2 <= (others => '0');
      end if;
      if RSSU = '1' then
        SUR <= (others => '0');
      end if;
      if LDT1 = '1' then
        TR1 <= TR1 + SUR;
      end if;
      if LDT2 = '1' then
        TR2 <= TR2 + SUR;
      end if;
      if ENADIE = '1' then
        case DIE is
          when "110" => DIE <= "001";
          when others => DIE <= DIE + 1;
        end case;
      end if;
    end if;
  end if;
end process;


```



```


if DIE = "001" then
  DIE1 <= '1';
else
  DIE1 <= '0';
end if;
if LDSU = '1' then
  SUR <= SUR + (frontbits & DIE);
end if;
if CP = '1' then
  D <= TR2;
else
  D <= TR1;
end if;
if (D > "1100011") then
  WN <= '1';
else
  WN <= '0';
end if;
end if;
--! connection to displays
LEDDIE <= DIE;
DIGIT0 <= bcd1;
DIGIT1 <= bcd2;
DIGIT2 <= bcd3;
DIGIT3 <= bcd4;
end process;

```

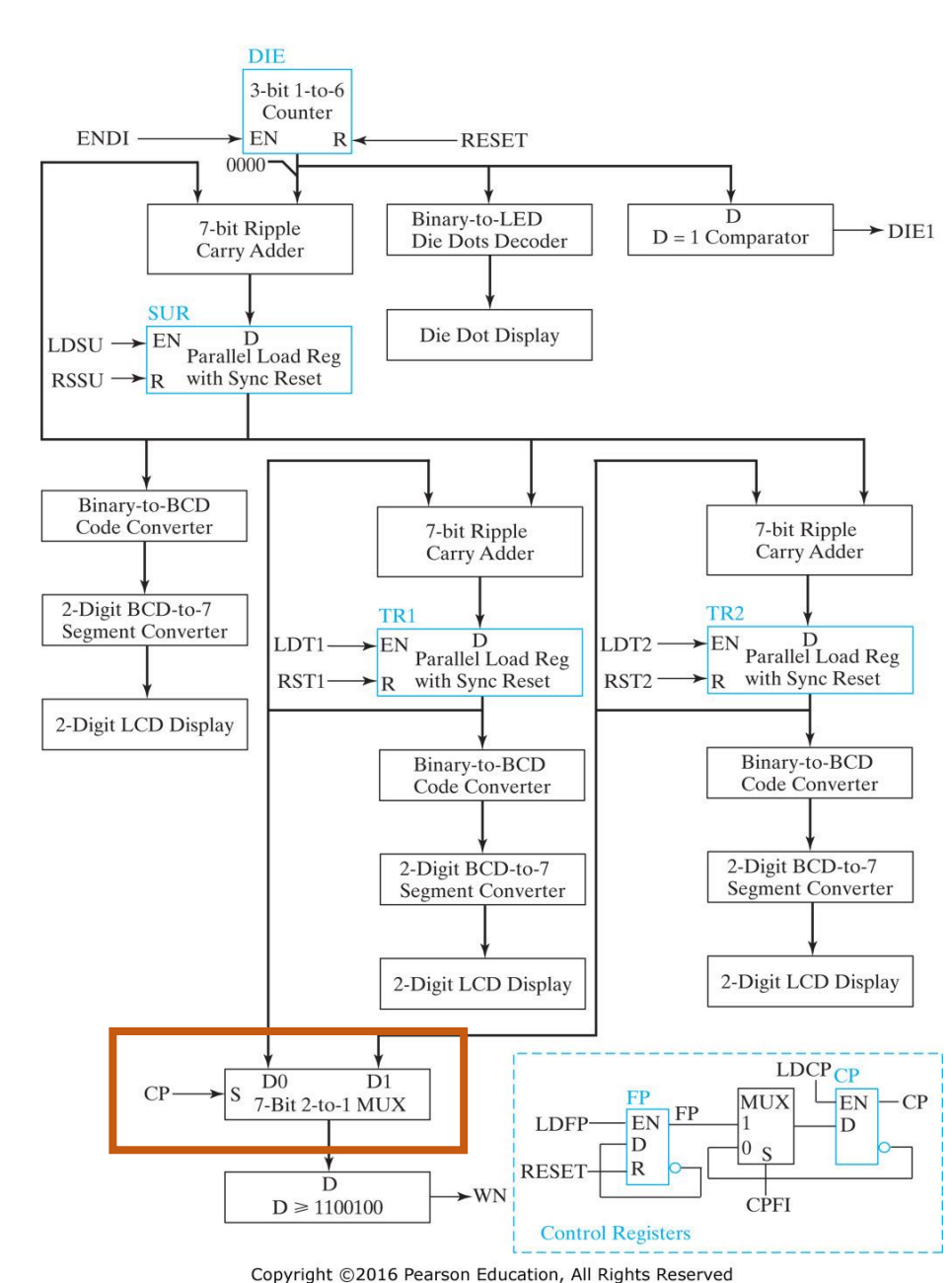




```
Main_process : process(clock,reset) begin
  if reset = '1' then
    -- reset
    DIE <= (others => '0'); --! asynchronous reset
  else
    if rising_edge(clock) then
      if RST1 = '1' then
        TR1 <= (others => '0');
      end if;
      if RST2 = '1' then
        TR2 <= (others => '0');
      end if;
      if RSSU = '1' then
        SUR <= (others => '0');
      end if;
      if LDT1 = '1' then
        TR1 <= TR1 + SUR;
      end if;
      if LDT2 = '1' then
        TR2 <= TR2 + SUR;
      end if;
      if ENADIE = '1' then
        case DIE is
          when "110" => DIE <= "001";
          when others => DIE <= DIE + 1;
        end case;
      end if;
    end if;
  end if;
end process;
```


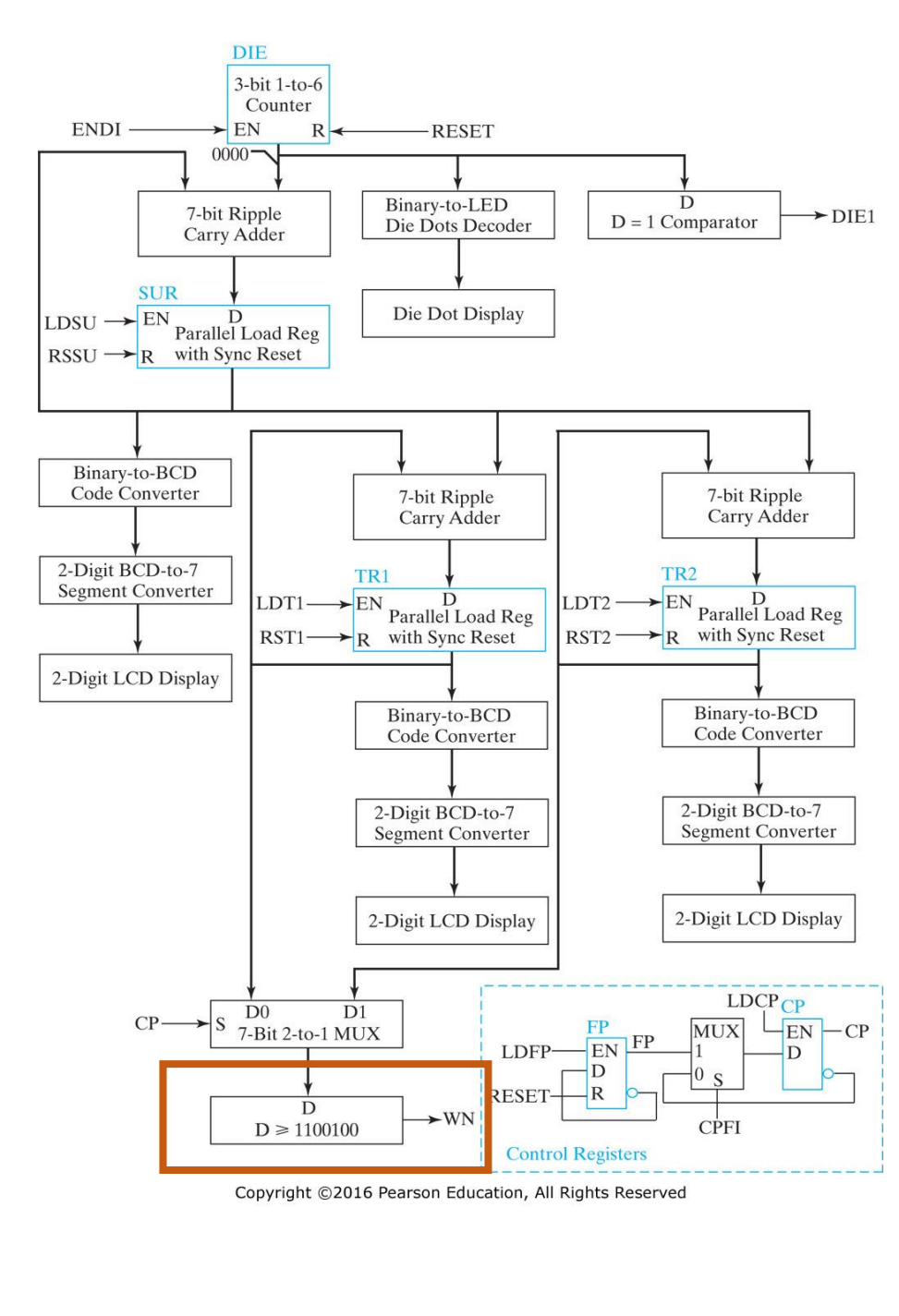
```
if DIE = "001" then
  DIE1 <= '1';
else
  DIE1 <= '0';
end if;
if LDSU = '1' then
  SUR <= SUR + (frontbits & DIE);
end if;
if CP = '1' then
  D <= TR2;
else
  D <= TR1;
end if;
if (D > "1100011") then
  WN <= '1';
else
  WN <= '0';
end if;
end if;
end if;
--! connection to displays
LEDDIE <= DIE;
DIGIT0 <= bcd1;
DIGIT1 <= bcd2;
DIGIT2 <= bcd3;
DIGIT3 <= bcd4;
end process;
```





entity controlunit is

port(

clock : in *std\_logic*; --! Clock

reset : in *std\_logic*; --! Reset

ROLL : in *std\_logic*; --! button for the roll

HOLD : in *std\_logic*; --! button for hold

NEWGAME: in *std\_logic*; --! button for new game

ENADIE : out *std\_logic*; --! Enable Die to increment

LDSU : out *std\_logic*; --! Add DIE to SUR register

LDT1 : out *std\_logic*; --! Add SUR to TR1 register

LDT2 : out *std\_logic*; --! Add SUR to TR2 register

RSSU : out *std\_logic*; --! Reset SUR register

RST1 : out *std\_logic*; --! Reset TR1 register

RST2 : out *std\_logic*; --! Reset TR2 register

BP1 : out *std\_logic*; --! enables blinking

CP : **inout** *std\_logic*; --! current player (register outside)

FP : **inout** *std\_logic*; --! First player (register outside)



DIE1 : in *std\_logic*; --! signal that the die is at one

WN : in *std\_logic* --! WIN has been achieved by a player

);

end entity controlunit;

## CONTROL UNIT

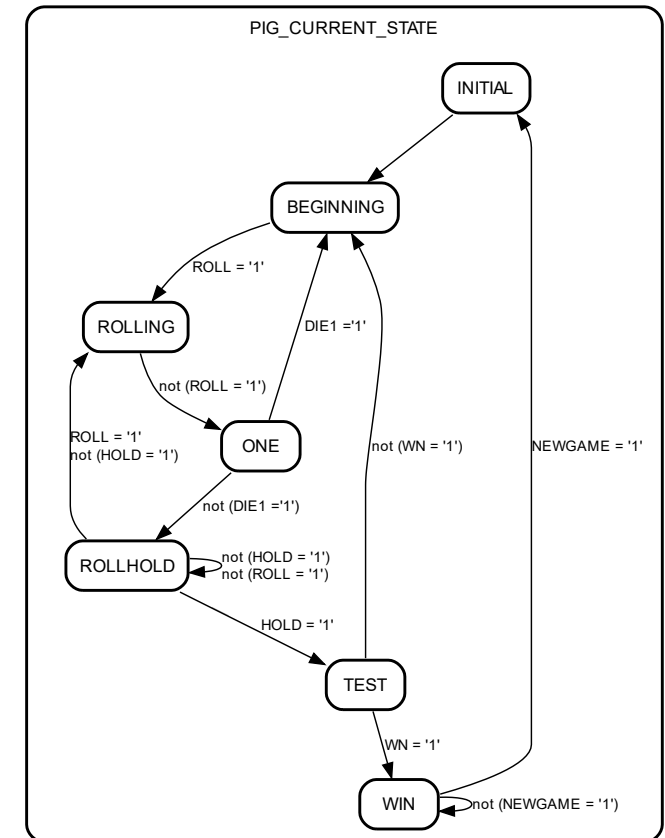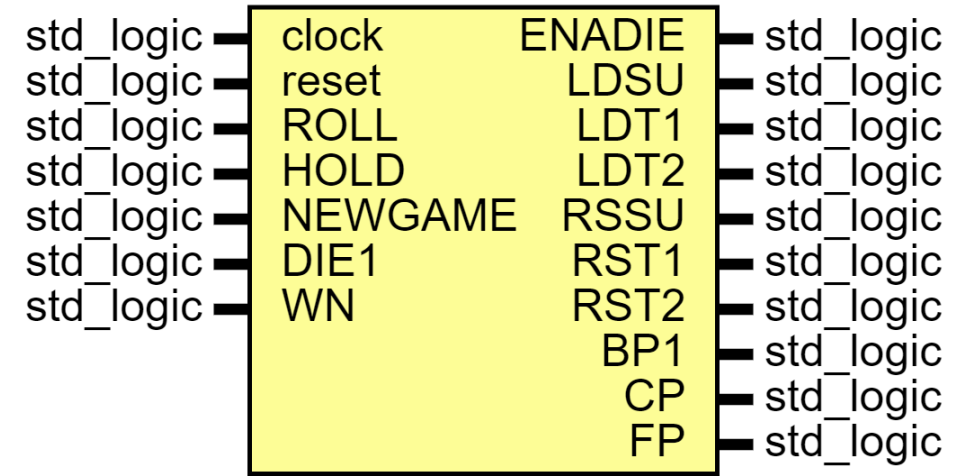

```

architecture rtl of controlunit is
    --type definition
    type PIG_STATE is (INITIAL, BEGINNING, ROLLING,
ONE, ROLLHOLD, TEST, WIN);
    --Signal definition
    signal PIG_CURRENT_STATE : PIG_STATE;
    begin
FSM : process(clock)
    begin
if rising_edge(clock) then
    if reset = '1' then --chosen this one but could
be anything to reset
        -- reset
        PIG_CURRENT_STATE <= INITIAL;
        FP <= '0';
    else
        --default values
        ENADIE <= '0';
        LDSU <= '0';
        LDT1 <= '0';
        LDT2 <= '0';
        RSSU <= '0';
        RST1 <= '0';
        RST2 <= '0';
        BP1 <= '0';

```

```

case PIG_CURRENT_STATE is
when INITIAL =>

        PIG_CURRENT_STATE <= BEGINNING;
        RST1 <= '1'; --! reset TR1
        RST2 <= '1'; --! reset TR2
        CP <= FP; --! behavioural implmentation

when BEGINNING =>
    RSSU <= '1';
        if ROLL = '1' then --! Press the button to roll
            PIG_CURRENT_STATE <= ROLLING;
        end if;
    when ROLLING =>

        if ROLL = '1' then
            ENADIE <= '1'; --! enables die increment
        else
            PIG_CURRENT_STATE <= ONE;
        end if;
    when ONE =>
        if DIE1 ='1' then
            CP <= not CP;
            PIG_CURRENT_STATE <= BEGINNING;
        else
            PIG_CURRENT_STATE <= ROLLHOLD;
            LDSU <= '1';
        end if;

```

```

when ROLLHOLD =>
    if HOLD = '1' then
        PIG_CURRENT_STATE <= TEST;
        CP <= not CP;
        if CP = '1' then
            LDT1 <= '1';
        else
            LDT2 <= '1';
        end if;
    else
        if ROLL = '1' then
            PIG_CURRENT_STATE <= ROLLING;
        else
            PIG_CURRENT_STATE <= ROLLHOLD;
        end if;
    end if;
end if;


```

```

when TEST =>
    if WN = '1' then
        PIG_CURRENT_STATE <= WIN;
    else
        PIG_CURRENT_STATE <= BEGINNING;
    end if;
    when WIN =>
        BP1 <= '1';
        if NEWGAME = '1' then
            FP <= not FP;
            PIG_CURRENT_STATE <= INITIAL;
        else
            PIG_CURRENT_STATE <= WIN;
        end if;
    end case;
end if;
end process;
end architecture ;

```

# Main

 

What's inside?